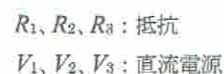


	V_{ab}	I_3
1	26 [V]	9 [A]
2	26 [V]	3 [A]
3	14 [V]	9 [A]
4	14 [V]	3 [A]



$$\boxed{I_1 + I_3 = I_2}$$

$$V_1 + V_2 = I_1 R_1 + I_2 R_2$$

$$V_2 + V_3 = I_2 R_2 + I_3 R_3$$

$$I_3 = 3A$$

$$20 - 6 = 4 = 14V$$

